



# Design and Analysis of Universality of NAND and NOR Gate, Synchronous Random Counters, 4-Bit Logic Units and Universal Logic Gates.

Presented by Tashnin Khan Tanisha (23201112), Nowrin Akhter Riya (23201117), Fahmida Tabassum (23201132), Fariya Rahman (23201136)

## Universality of NAND and NOR Gate

This experiment highlights how NAND and NOR gate perform all basic logic operations, establishing their universality in digital logic circuit design .

- Did you know?  
Every digital device we use from calculator to computers! Is built using universal gates like NAND and NOR!
- All logic operations-AND,OR,NOT can be built using just NAND or NOR gates. Universality at it's finest!

### TRUTH TABLE

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

AND


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

OR

A	Y
0	1
1	0

NOT

### CIRCUIT DIAGRAM

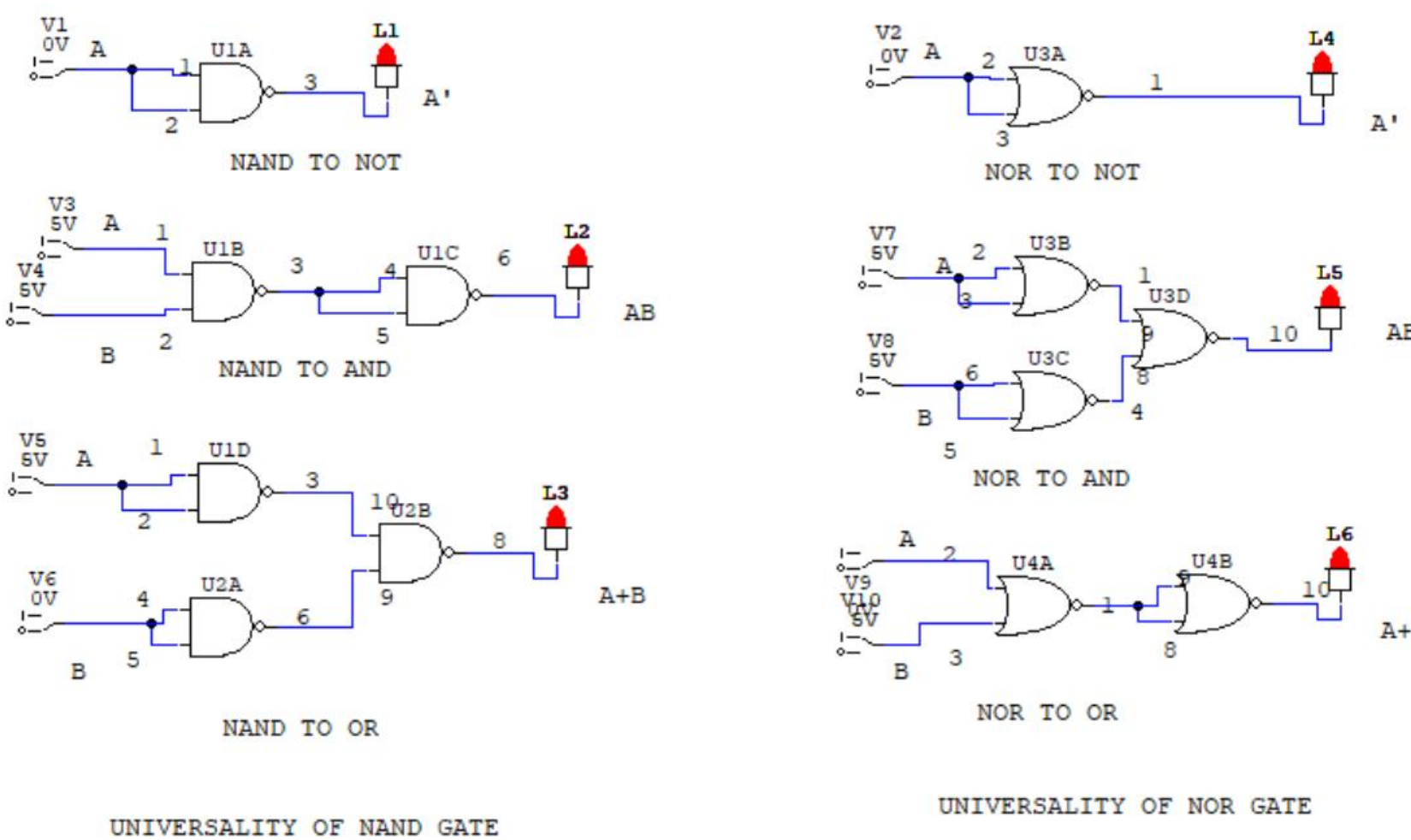

- AND waits for both 1s
  - OR needs just one
  - NOT loves to flip the game
- From truth tables to glowing results the power of universal gates!

## Synchronous Random Counter


A 5-bit synchronous counter that counts even numbers -30, 28, 26, 24, 22, 20, 18, 16, 14, 12, 10, 8, 6, 4, 2, 0., step by step, in reverse!

- Each clock pulse brings a perfectly timed descent in the digital sequence. Precision, control, and rhythm — that's synchronous logic in action!
- Configure the flip-flops — JA=0, KA=0; JB=B', KB=B; JC=B'C', KC=B'C; JD=B'C'D', KD=B'C'D; JE=B'C'D'E', KE=B'C'D'E., And watch it do wonders!


### TRUTH TABLE

Q1	Qn	J	K
	+1		
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

### CIRCUIT DIAGRAM

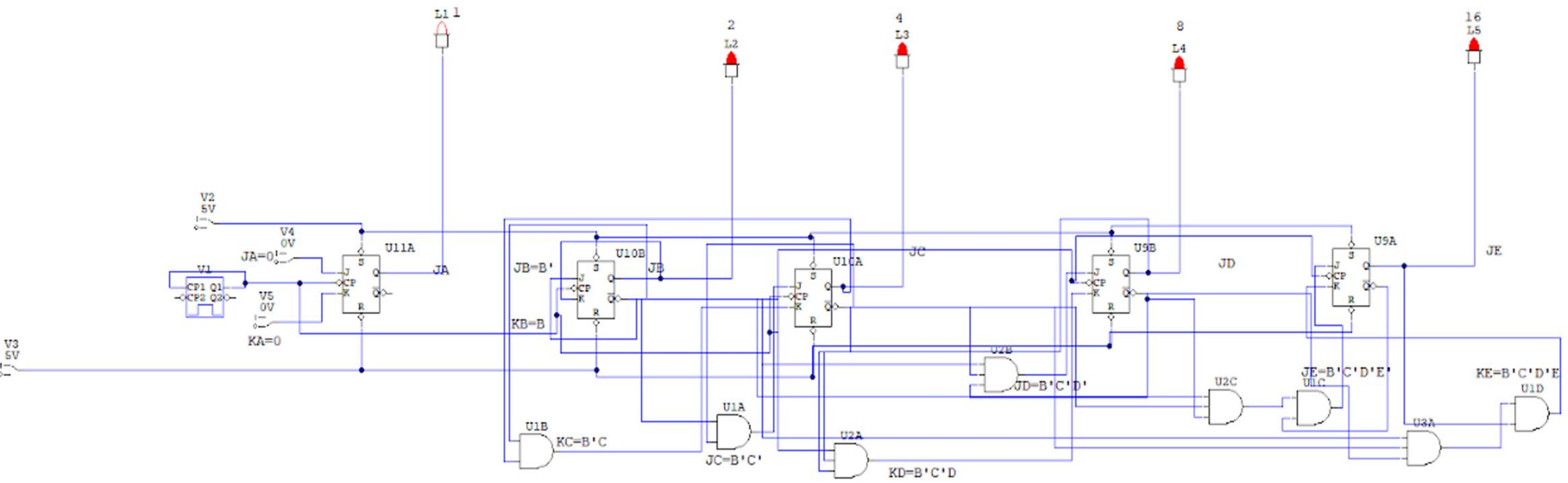

Tick. Flip. Repeat.

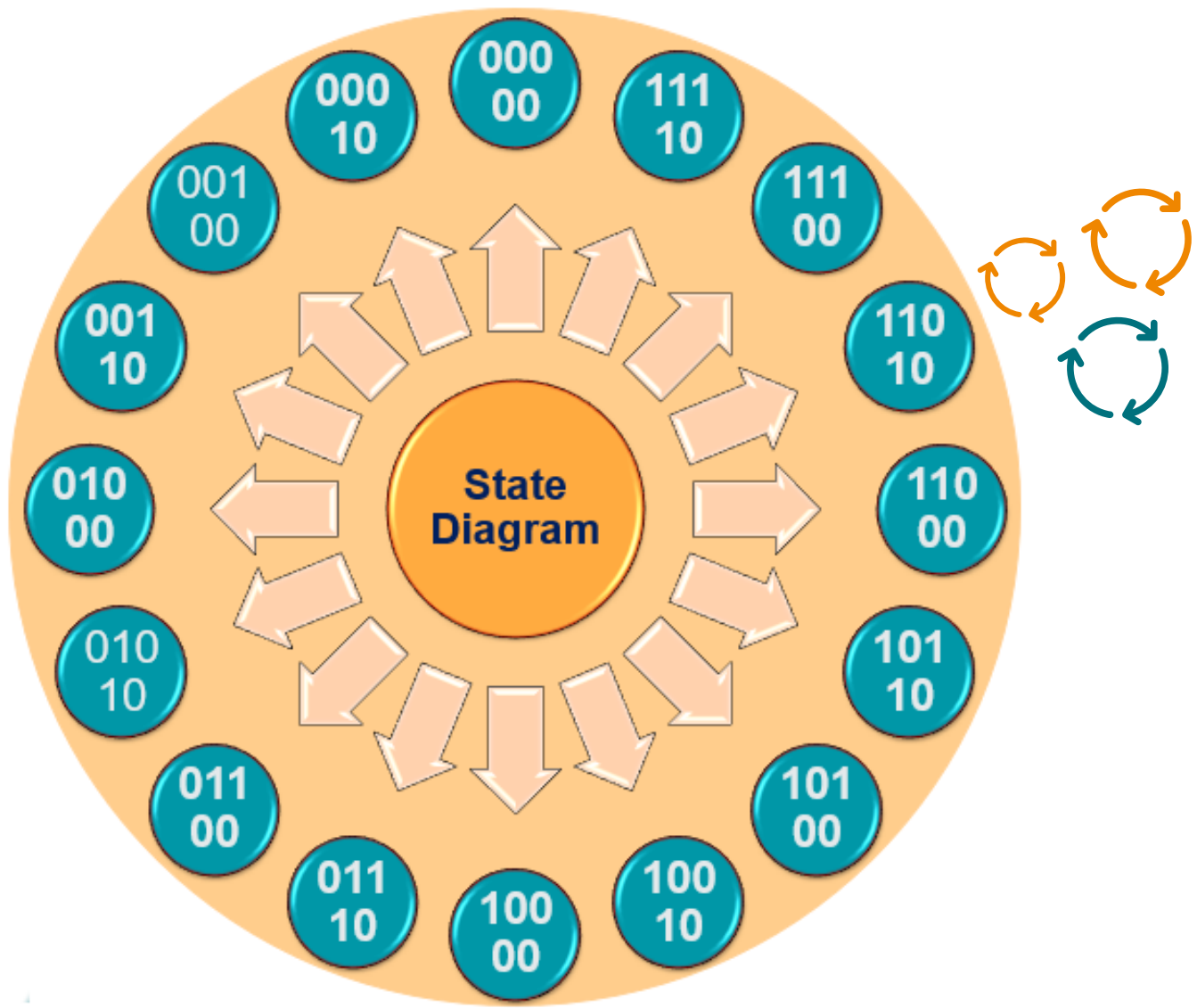

## 4-Bit Logic Units and Universal Logic Gates


- This experiment demonstrates a 4-bit logic unit where AND,OR,NOT and XOR operations are implemented using multiplexers (MUX),showing how MUX can be used to realize multiple logic functions efficiently.
- This unit emphasizes the role of MUX is simplifying and optimizing digital circuits. It highlights modularity, versatility, and compactness in digital circuit design.

### TRUTH TABLE

S1	S2	Q
0	0	I0
0	1	I1
1	0	I2
1	1	I3

- S1 = 0, S2 = 0 → AND: Boom! It's AND!
- S1 = 0, S2 = 1 → OR: Flip the switch, it's OR!
- S1 = 1, S2 = 0 → NOT: Invert and there you go, NOT!
- S1 = 1, S2 = 1 → XOR: Two inputs differ? That's XOR!

### CIRCUIT DIAGRAM

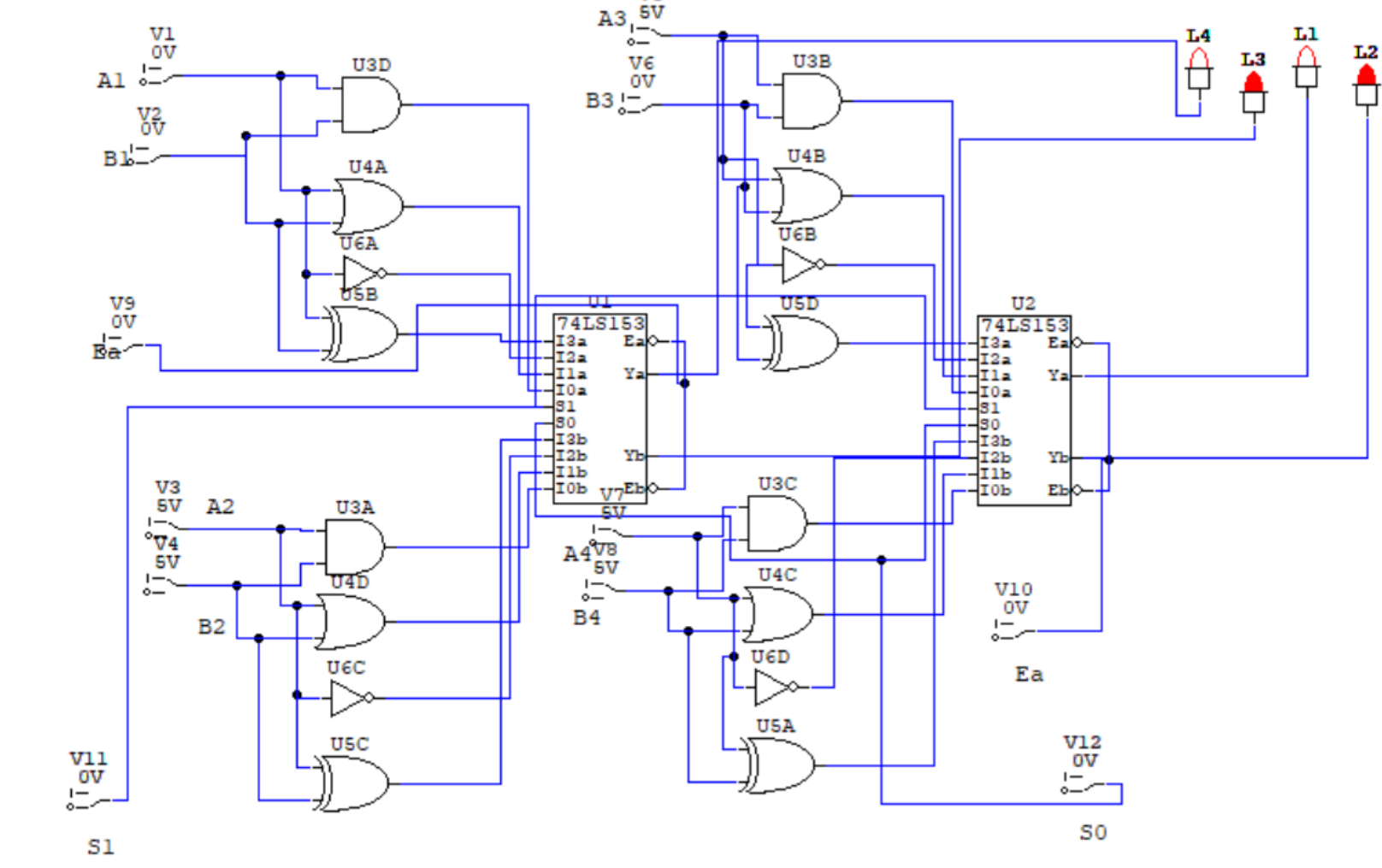

1	Ea	VCC	16
2	S1	Eb'	15
3	I3a	S0	14
4	I2a	I3b	13
5	I1a	I2b	12
6	I0a	I1b	11
7	Ya	I0b	10
8	GND	Yb	9

PIN CONFIGURATION